

CS61C - Machine Structures

Lecture 20 - Datapath

November 8, 2000

David Patterson

<http://www-inst.eecs.berkeley.edu/~cs61c/>

CS61C L20 Datapath © UC Regents

1

Review 1/3

- Apply Principle of Locality Recursively
- Reduce Miss Penalty? add a (L2) cache
- Manage memory to disk? Treat as cache
 - Included protection as bonus, now critical
 - Use **Page Table** of mappings vs. tag/data in cache
- Virtual memory to Physical Memory Translation too slow?
 - Add a cache of Virtual to Physical Address Translations, called a **TLB**

CS61C L20 Datapath © UC Regents

2


Review 2/3

- Virtual Memory allows protected sharing of memory between processes with less swapping to disk, less fragmentation than always swap or base/bound
- Spatial Locality means Working Set of Pages is all that must be in memory for process to run fairly well
- TLB to reduce performance cost of VM
- Need more compact representation to reduce memory size cost of simple 1-level page table (especially 32- ⇒ 64-bit address)

CS61C L20 Datapath © UC Regents

3

Review 3/3: Paging/Virtual Memory

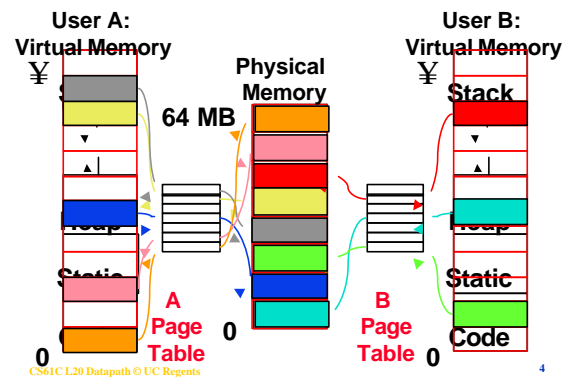

CS61C L20 Datapath © UC Regents

4


Outline

- Datapath Walkthroughs
- Hardware Building Blocks
- ALU Design
- Full Adder
- Datapath utilization

CS61C L20 Datapath © UC Regents

5

Five Components of a Computer

 

CS61C L20 Datapath © UC Regents

6

The CPU

- **Processor (CPU)**: the active part of the computer, which does all the work (data manipulation and decision-making)
- **Datapath**: portion of the processor which contains hardware necessary to perform all operations required by the computer (the brawn)
- **Control**: portion of the processor (also in hardware) which tells the datapath what needs to be done (the brain)

CS61C L20 Datapath © UC Regents

7

Stages of the Datapath (1/6)

- **Problem**: a single, atomic block which “executes an instruction” (performs all necessary operations beginning with fetching the instruction) would be too bulky and inefficient
- **Solution**: break up the process of “executing an instruction” into stages, and then connect the stages to create the whole datapath
 - smaller stages are easier to design
 - easy to optimize (change) one stage without touching the others

CS61C L20 Datapath © UC Regents

8

Stages of the Datapath (2/6)

- There is a *wide* variety of MIPS instructions: so what general steps do they have in common?
- **Stage 1: Instruction Fetch**
 - no matter what the instruction, the 32-bit instruction word must first be fetched from memory (the cache-memory hierarchy)
 - also, this is where we **Increment PC** (that is, $PC = PC + 4$, to point to the next instruction: byte addressing $so + 4$)

CS61C L20 Datapath © UC Regents

9

Stages of the Datapath (3/6)

- **Stage 2: Instruction Decode**
 - upon fetching the instruction, we next gather data from the fields (*decode* all necessary instruction data)
 - first, read the Opcode to determine instruction type and field lengths
 - second, read in data from all necessary registers
 - for `add`, read two registers
 - for `addi`, read one register
 - for `jal`, no reads necessary

CS61C L20 Datapath © UC Regents

10

Stages of the Datapath (4/6)

- **Stage 3: ALU (Arithmetic-Logic Unit)**
 - the real work of most instructions is done here: arithmetic (`+`, `-`, `*`, `/`), shifting, logic (`&`, `|`), comparisons (`slt`)
 - what about loads and stores?
 - `lw $t0, 40($t1)`
 - the address we are accessing in memory = the value in `$t1` PLUS the value 40
 - so we do this addition in this stage

CS61C L20 Datapath © UC Regents

11

Stages of the Datapath (5/6)

- **Stage 4: Memory Access**
 - actually only the load and store instructions do anything during this stage; the others remain idle
 - since these instructions have a unique step, we need this extra stage to account for them
 - as a result of the cache system, this stage is expected to be just as fast (on average) as the others

CS61C L20 Datapath © UC Regents

12

Stages of the Datapath (6/6)


◦ Stage 5: Register Write

- most instructions write the result of some computation into a register
- examples: arithmetic, logical, shifts, loads, `slt`
- what about stores, branches, jumps?
 - don't write anything into a register at the end
 - these remain idle during this fifth stage

CS61C L20 Datapath © UC Regents

13

Generic Steps=> Datapath

 

CS61C L20 Datapath © UC Regents

14

Datapath Walkthroughs (1/3)


◦ `add $r3,$r1,$r2 # r3 = r1+r2`

- Stage 1: fetch this instruction, inc. PC
- Stage 2: decode to find it's an `add`, then read registers `$r1` and `$r2`
- Stage 3: add the two values retrieved in Stage 2
- Stage 4: idle (nothing to write to memory)
- Stage 5: write result of Stage 3 into register `$r3`

CS61C L20 Datapath © UC Regents

15

Example: ADD Instruction

 

CS61C L20 Datapath © UC Regents

16

Datapath Walkthroughs (2/3)


◦ `slti $r3,$r1,17`

- Stage 1: fetch this instruction, inc. PC
- Stage 2: decode to find it's an `slti`, then read register `$r1`
- Stage 3: compare value retrieved in Stage 2 with the integer 17
- Stage 4: go idle
- Stage 5: write the result of Stage 3 in register `$r3`

CS61C L20 Datapath © UC Regents

17

Example: SLTI Instruction

 

CS61C L20 Datapath © UC Regents

18


Datapath Walkthroughs (3/3)

- `sw $r3, 17($r1)`
 - Stage 1: fetch this instruction, inc. PC
 - Stage 2: decode to find it's a `sw`, then read registers `$r1` and `$r3`
 - Stage 3: add 17 to value in register `$r1` (retrieved in Stage 2)
 - Stage 4: write value in register `$r3` (retrieved in Stage 2) into memory address computed in Stage 3
 - Stage 5: go idle (nothing to write into a register)

CS61C L20 Datapath © UC Regents

19

Example: SW Instruction

 

CS61C L20 Datapath © UC Regents

20


Administrivia

- Homework 8 (next week)
 - Want to fill in page tables to learn material, so easiest way is to turn in paper; no electronic submission
- Grading scale (same as Spring 99, Fall 99)
 - 95% A+, 90% A, 85% A-, 80% B+, 75% B, 70% B-, 65% C+, 60% C, 55% C-, 45% D

CS61C L20 Datapath © UC Regents

21

Survey

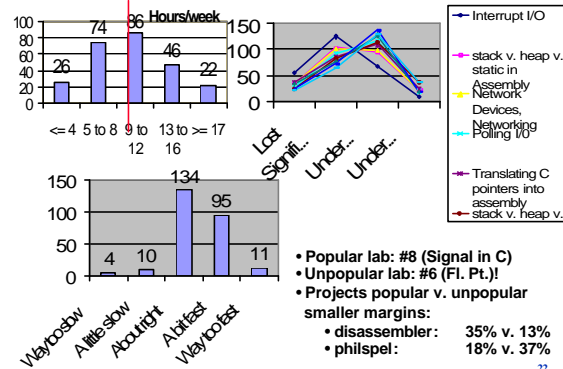

CS61C L20 Datapath © UC Regents

21

Why Five Stages? (1/2)

- Could we have a different number of stages?
 - Yes, and other architectures do
- So why does MIPS have five if instructions tend to go idle for at least one stage?
 - There is one instruction that uses all five stages: the load

CS61C L20 Datapath © UC Regents

23


Why Five Stages? (2/2)

- `lw $r3, 17($r1)`
 - Stage 1: fetch this instruction, inc. PC
 - Stage 2: decode to find it's a `lw`, then read register `$r1`
 - Stage 3: add 17 to value in register `$r1` (retrieved in Stage 2)
 - Stage 4: read value from memory address compute in Stage 3
 - Stage 5: write value found in Stage 4 into register `$r3`

CS61C L20 Datapath © UC Regents

24

Example: LW Instruction

 


What Hardware Is Needed? (1/2)

- ° PC: a register which keeps track of VA of the next instruction
- ° General Purpose Registers
 - used in Stages 2 (Read) and 5 (Write)
 - we're currently working with 32 of these
- ° Memory
 - used in Stages 1 (Fetch) and 4 (R/W)
 - cache system makes these two stages as fast as the others, on average

Datapath Summary

 - ° Construct datapath based on register transfers required to perform instructions
- ° Control part causes the right transfers to happen



What Hardware Is Needed? (2/2)

- ° ALU
 - used in Stage 3
 - something that performs all necessary types of work: arithmetic, logicals, etc.
 - we'll design this later
- ° Miscellaneous Registers
 - hold intermediate data, such as results in between stages, etc.
 - Note: Register is a general purpose term meaning something that stores bits.

Hardware Building Blocks (1/6)

- ° In reality, CPUs are built out of transistors and wires (plus resistors and capacitors).
- ° For this class, we'll do design using **gates** and **wires**.
- ° Gate:
 - hardware unit that receives a certain number of inputs and produces one output: implements one of the basic logic functions
 - can be represented as a truth table
 - actually implemented in transistors

Hardware Building Blocks (2/6)

AND Gate

Symbol


Definition *called a "truth table"*

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

- ° We can have more inputs:
 - C = 1 if and only if ALL inputs are 1

Hardware Building Blocks (3/6)

OR Gate

 

Definition

A	B	C
0	0	0
0	1	1
1	0	1
1	1	1

◦ We can have more inputs:


- C = 1 if and only if ANY input is 1

CS61C L20 Datapath © UC Regents

31

Hardware Building Blocks (4/6)

Inverter

 

Definition

A	C
0	1
1	0

◦ In this case, there is always exactly one input and one output.


◦ Note: Inverter is usually drawn as just a bubble, without the triangle.

CS61C L20 Datapath © UC Regents

32

Hardware Building Blocks (5/6)

Multiplexor (MUX)

 

Definition

D	C
0	A
1	B

CS61C L20 Datapath © UC Regents

33

Hardware Building Blocks (6/6)

◦ General Muxes:

- have control bits and data bits
- control bits select which data bit will pass through: all others are blocked
- in general,
 - 1 control bit selects between 2 data bits,
 - 2 control bits select between 4 data bits,
 - 3 control bits select between 8 data bits,
 - n control bits select between 2^n data bits
- so we can build a mux of any size to serve our purpose

CS61C L20 Datapath © UC Regents

34

Registers

◦ General Definition of a Register

- a place where we can store one or more bits for future retrieval
- since registers are in hardware, they can be designed using gates and wires

◦ In MIPS, we have:

- 32 general purpose registers used by programs for computations
- registers in the datapath used to store data between Stages
- a few more (such as PC, hi, lo)

CS61C L20 Datapath © UC Regents

35

ALU Design Philosophies (1/4)

◦ Fact: All basic hardware building blocks accept individual bits at inputs and output individual bit.

◦ Fact: The MIPS ALU (generally) needs to work with 32-bit registers.

◦ Design Philosophy #1: For simplicity, build 32 separate one-bit ALUs, and then figure out what needs to be done to connect them.

CS61C L20 Datapath © UC Regents

36

ALU Design Philosophies (2/4)

- Fact: ALU needs to perform a *WIDE* variety of tasks: add, subtract, multiply, divide, shift, compare, etc.
- Design Philosophy #2:
 - Build separate hardware blocks for each necessary task.
 - When inputs come in, perform all possible operations in parallel.
 - Use a **mux** to choose which operation is actually desired.
 - Note: Since everything's done in parallel, no time is lost.

ALU Design Philosophies (3/4)


- Consequence of Design Philosophy #2:
 - New operations can be added to the ALU just by adding new data lines into the muxes and informing Control of the change.
 - This means that new instructions can be added to the system without changing everything: just a small portion of the ALU.

ALU Design Philosophy (4/4)

- There will be more places in the design where we need to make a decision:
 - so feel free to add a mux whenever necessary
 - assume that control signals for all muxes can be handled by the Control

In the Beginning

 
- The ALU consists of 32 muxes (one for each necessary output bit).



- Now we go through instruction set and add data lines to implement all necessary functionality.

Logical Instructions (1/2)

 - AND instruction
 - one of data lines should be a simple AND gate
- OR instruction
 - another data line should be a simple OR gate




One-Bit Full Adder (1/3)

- Example Binary Addition:


a:	0	0	1	1	Carries
b:	0	1	0	1	
Sum:	1	0	0	0	

- Thus for any bit of addition:
 - The inputs are a_i , b_i , $CarryIn_i$
 - The outputs are Sum_i , $CarryOut_i$
 - Note: $CarryIn_{i+1} = CarryOut_i$

One-Bit Full Adder (2/3)

 

Add 1-bit Adder to 1-bit ALU

 

° Now connect 32 1-bit ALUs together


One-Bit Full Adder (3/3)

- ° To create one-bit full adder:
 - implement gates for Sum
 - implement gates for CarryOut
 - connect all inputs with same name
 - the symbol for one-bit full adder now represents this jumble of gates and wires (simplifies schematics)

Constructing Hardware to Match Definition

- ° Given any table of binary inputs for a binary output, programs can automatically connect a minimal number of AND gates, OR gates, and Inverters to produce the desired function
- ° Such programs generically called “Computer Aided Design”, or CAD

Example: HW gates for CarryOut

 

° Gates for Sum left as exercise to Reader

Things to Remember (1/3)

- ° Datapath is the hardware that performs operations necessary to execute programs.
- ° Control instructs datapath on what to do next.
- ° Datapath needs:
 - access to storage (general purpose registers and memory)
 - computational ability (ALU)
 - helper hardware (local registers and PC)

Things to Remember (2/3)

- Five stages of datapath (executing an instruction):
 1. Instruction Fetch (Increment PC)
 2. Instruction Decode (Read Registers)
 3. ALU (Computation)
 4. Memory Access
 5. Write to Registers
- ALL instructions must go through ALL five stages.
- Datapath designed in hardware.

Things to Remember (3/3)

- When inputs come into ALU stage, all possible calculations/operations are performed on them.
- One big mux then chooses which operation is actually desired.
- New functionality can be added simply by modifying the existing ALU (adding a new data line to the mux, if necessary)
- Computer Aided Design can create gates to implement function defined in any truth table