CS 152 Computer Architecture and Engineering

Lecture 10: Designing a Multicycle Processor

October 1, 1997

Dave Patterson (http.cs.berkeley.edu/~patterson)

lecture slides: http://www-inst.eecs.berkeley.edu/~cs152/

DAP Fa97, © U.CB

Recap: Processor Design is a Process

- Bottom-up
  - assemble components in target technology to establish critical timing
- Top-down
  - specify component behavior from high-level requirements
- Iterative refinement
  - establish partial solution, expand and improve

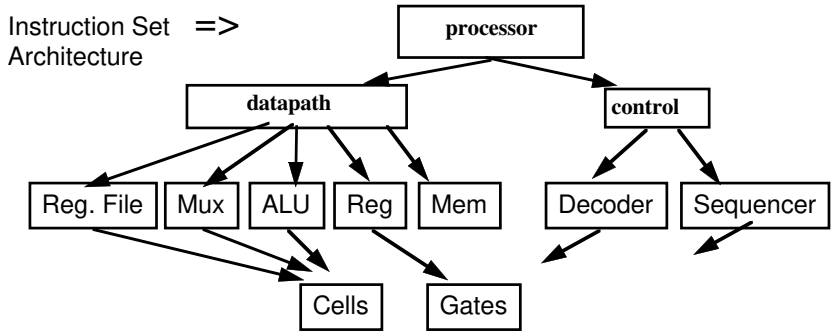

DAP Fa97, © U.CB

Recap: A Single Cycle Datapath

- We have everything except control signals (underline)
  - Today's lecture will show you how to generate the control signals

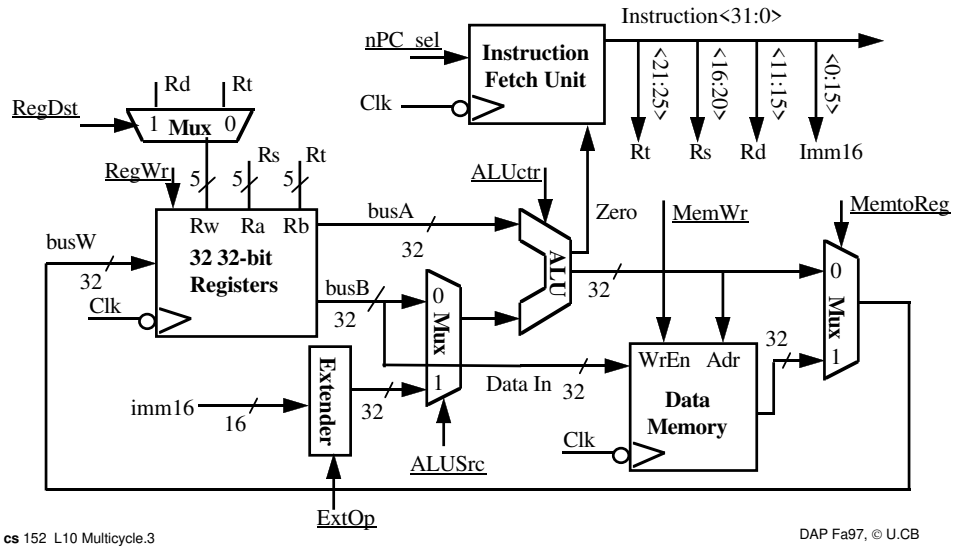

DAP Fa97, © U.CB

Recap: The "Truth Table" for the Main Control

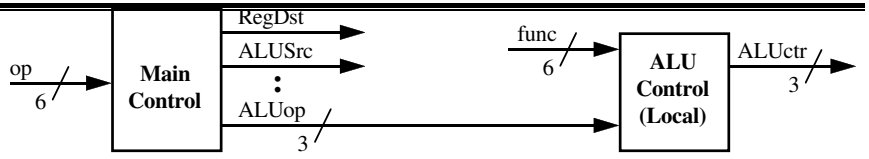

op	00 0000	00 1101	10 0011	10 1011	00 0100	00 0010
	R-type	**ori**	**lw**	**sw**	**beq**	**jump**
RegDst	1	0	0	x	x	x
ALUSrc	0	1	1	1	0	x
MemtoReg	0	0	1	x	x	x
RegWrite	1	1	1	0	0	0
MemWrite	0	0	0	1	0	0
Branch	0	0	0	0	1	0
Jump	0	0	0	0	0	1
ExtOp	x	0	1	1	x	x
ALUop (Symbolic)	"R-type"	Or	Add	Add	Subtract	xxx
ALUop <2>	1	0	0	0	0	x
ALUop <1>	0	1	0	0	0	x
ALUop <0>	0	0	0	0	1	x

DAP Fa97, © U.CB

Recap: PLA Implementation of the Main Control

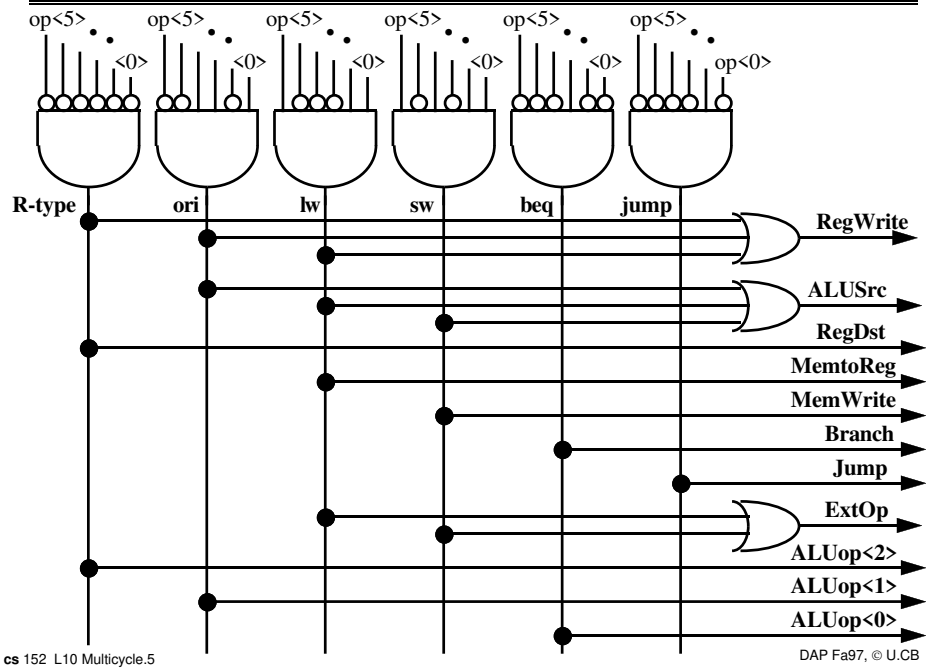

DAP Fa97, © U.CB

Recap: Systematic Generation of Control

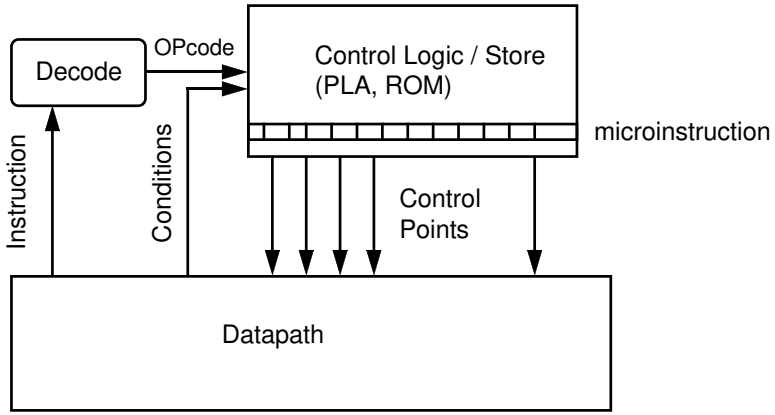

- In our single-cycle processor, each instruction is realized by exactly one control command or "*microinstruction*"
  - in general, the controller is a finite state machine
  - microinstruction can also control sequencing (see later)

DAP Fa97, © U.CB

The Big Picture: Where are We Now?

- The Five Classic Components of a Computer

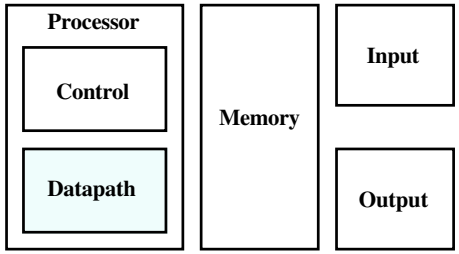

- Today's Topic: Designing the Datapath for the Multiple Clock Cycle Datapath

DAP Fa97, © U.CB

Outline of Today's Lecture

- Recap: single cycle processor
- VHDL versions
- Faster designs
- Multicycle Datapath
- Performance Analysis
- Multicycle Control

DAP Fa97, © U.CB

Behavioral models of Datapath Components

```
entity adder16 is
generic (ccOut_delay : TIME := 12 ns;
        adderOut_delay:  TIME := 12 ns);
port(A, B:     in  vlbit_1d(15  downto 0);
    DOUT:      out vlbit_1d(15 downto 0);
    CIN:    in vlbit;
    COUT:      out vlbit);
end adder16;
```

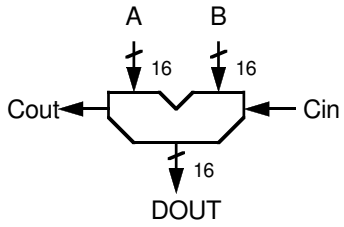


```
architecture behavior of adder32 is
begin
        adder16_process: process(A, B, CIN)

        variable tmp    : vlbit_1d(18 downto 0);
        variable adder_out : vlbit_1d(31 downto 0);
        variable carry: vlbit;

        begin
            tmp := addum (addum (A, B), CIN);
            adder_out := tmp(15 downto 0);
            carry :=tmp(16);

            COUT <= carry after ccOut_delay;
            DOUT <= adder_out after adderOut_delay;
        end process;
end behavior;
```


DAP Fa97, © U.CB

Behavioral Specification of Control Logic

```
entity maincontrol  is
port(opcode:        in  vlbit_1d(5 downto 0);
     equal_cond:    in vlbit;

      extop         out vlbit;
      ALUsrc        out vlbit;
      ALUop         out vlbit_1d(1 downto 0);
      MEMwr         out vlbit;
      MemtoReg      out vlbit;
      RegWr         out vlbit;
      RegDst        out vlbit;
      nPC           out vlbit;
end maincontrol;
```

 

- Decode / Control-store address modeled by Case statement
- Each arm drives control signals for that operation
  - just like the microinstruction
  - either can be symbolic

DAP Fa97, © U.CB

Abstract View of our single cycle processor

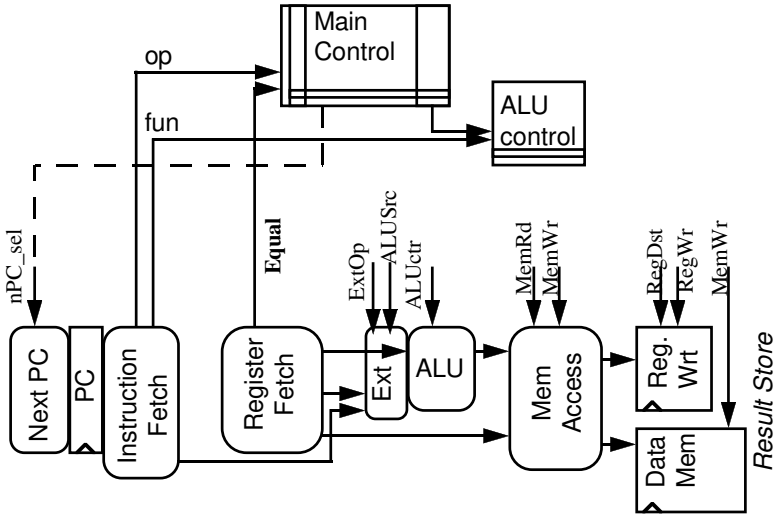

- looks like a FSM with PC as state

DAP Fa97, © U.CB

What's wrong with our CPI=1 processor?

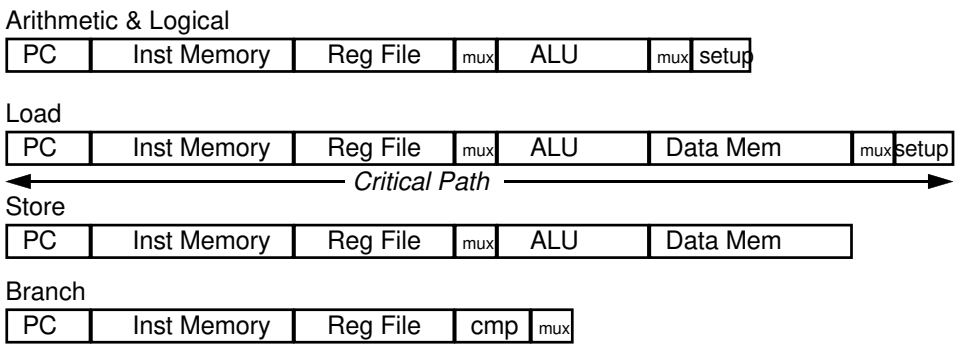

- Long Cycle Time
- All instructions take as much time as the slowest
- Real memory is not so nice as our idealized memory
  - cannot always get the job done in one (short) cycle

DAP Fa97, © U.CB

Memory Access Time

- **Physics => fast memories are small (large memories are slow)**

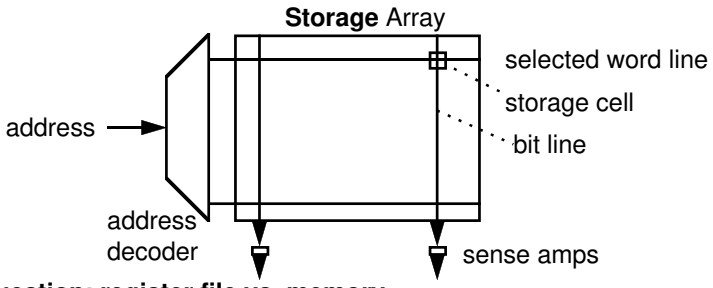

  - **question: register file vs. memory**

- **=> Use a hierarchy of memories**

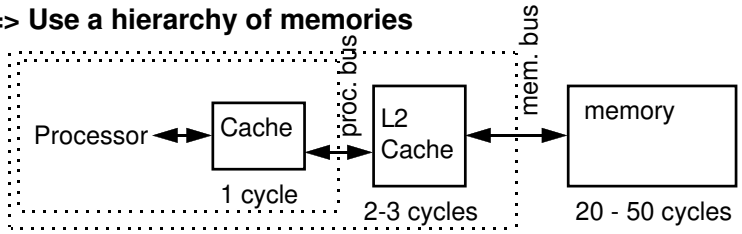

DAP Fa97, © U.CB

Reducing Cycle Time

- **Cut combinational dependency graph and insert register / latch**
- **Do same work in two fast cycles, rather than one slow one**

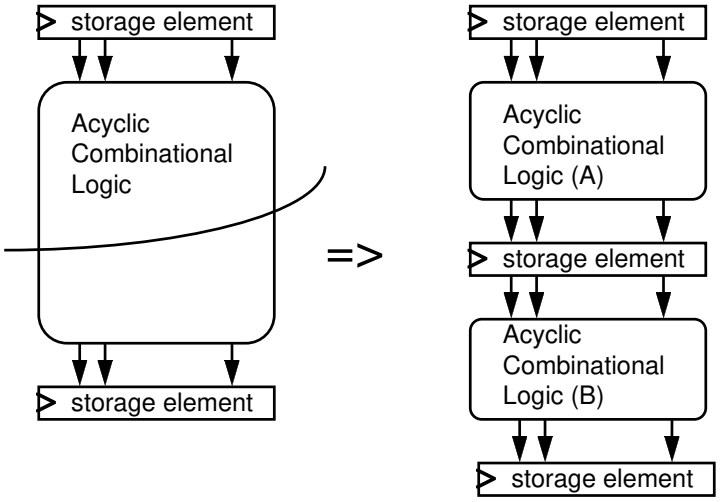

DAP Fa97, © U.CB

Basic Limits on Cycle Time

- **Next address logic**
  - **PC <= branch ? PC + offset : PC + 4**
- **Instruction Fetch**
  - **InstructionReg <= Mem[PC]**
- **Register Access**
  - **A <= R[rs]**
- **ALU operation**
  - **R <= A + B**

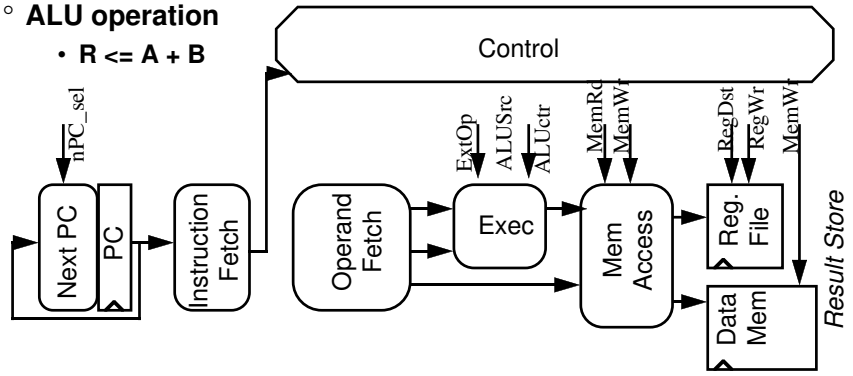

DAP Fa97, © U.CB

Partitioning the CPI=1 Datapath

- **Add registers between smallest steps**

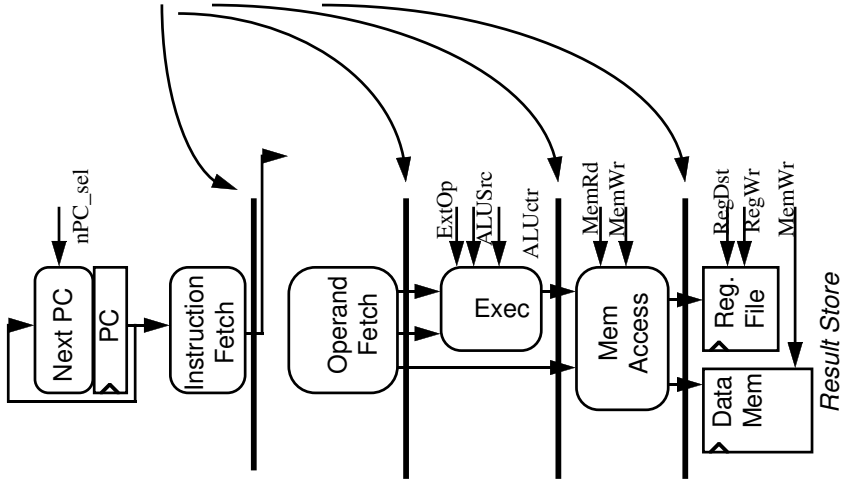

DAP Fa97, © U.CB

Example Multicycle Datapath

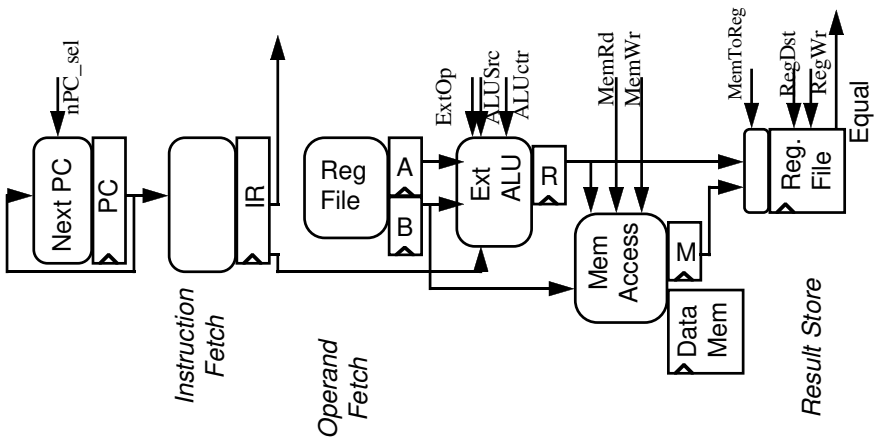

° Critical Path ?

DAP Fa97, © U.CB

Administrative Issues

° Read Chapter 5

° This lecture and next one slightly different from the book

° Midterm next Wednesday 10/8/97:
- 5:30pm to 8:30pm, 306 Soda
- No class on that day

° Midterm reminders:
- Pencil, calculator, one 8.5" x 11" (both sides) of handwritten notes
- Sit in every other chair, every other row (odd row & odd seat)

° Meet at LaVal's pizza after the midterm

DAP Fa97, © U.CB

Recall: Step-by-step Processor Design

Step 1: ISA => Logical Register Transfers

Step 2: Components of the Datapath

Step 3: RTL + Components => Datapath

Step 4: Datapath + Logical RTs => Physical RTs

Step 5: Physical RTs => Control

DAP Fa97, © U.CB

Step 4: R-rtype (add, sub, . . .)

° Logical Register Transfer

inst	Logical Register Transfers
ADDU	R[rd] <– R[rs] + R[rt]; PC <– PC + 4

° Physical Register Transfers

inst	Physical Register Transfers
	IR <– MEM[pc]
ADDU	A<– R[rs]; B <– R[rt]
	S <– A + B
	R[rd] <– S; PC <– PC + 4

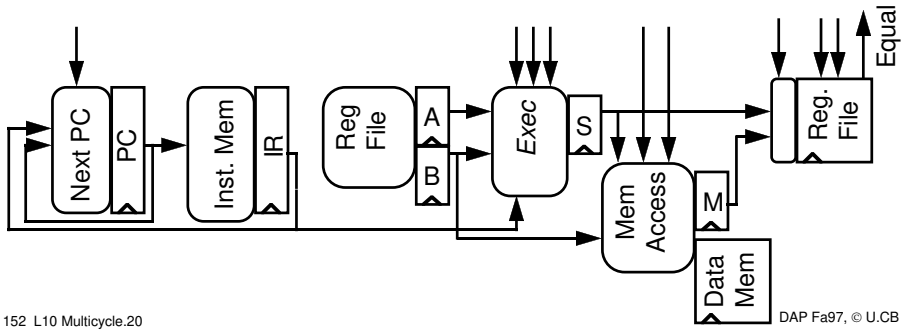

DAP Fa97, © U.CB

Step 4:Logical immed

- Logical Register Transfer

inst	Logical Register Transfers
ADDU	R[rt] <– R[rs] OR zx(Im16); PC <– PC + 4

- Physical Register Transfers

inst	Physical Register Transfers
	IR <– MEM[pc]
ADDU	A<– R[rs]; B <– R[rt]
	S <– A *or* ZeroExt(Im16)
	R[rt] <– S; PC <– PC + 4

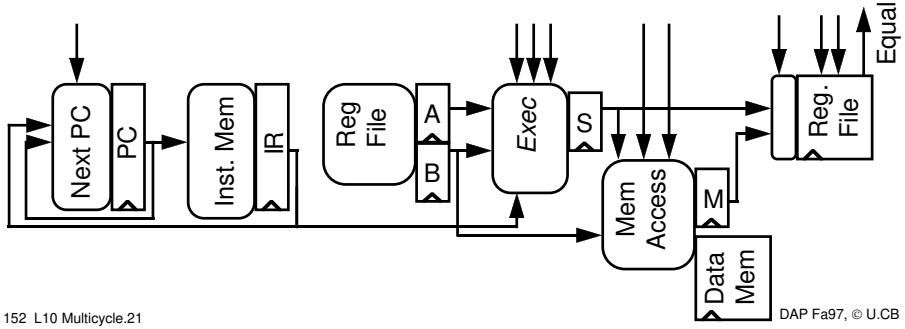

DAP Fa97, © U.CB

Step 4 : Load

- Logical Register Transfer

inst	Logical Register Transfers
LW	R[rt] <– MEM(R[rs] + sx(Im16); PC <– PC + 4

- Physical Register Transfers

inst	Physical Register Transfers
	IR <– MEM[pc]
LW	A<– R[rs]; B <– R[rt]
	S <– A + SignEx(Im16)
	M <– MEM[S]
	R[rd] <– M; PC <– PC + 4

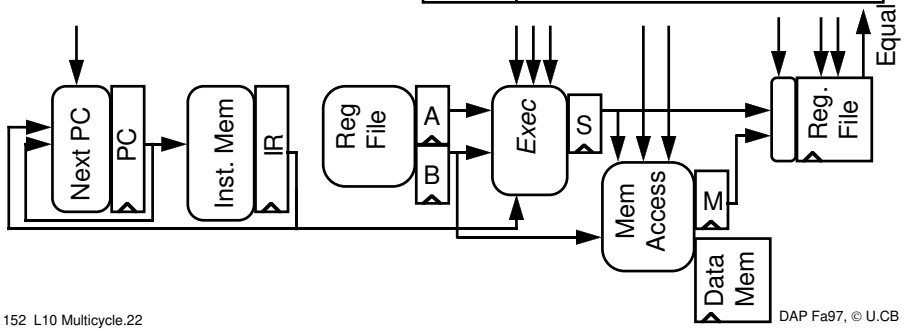

DAP Fa97, © U.CB

Step 4 : Store

- Logical Register Transfer

inst	Logical Register Transfers
SW	MEM(R[rs] + sx(Im16) <– R[rt]; PC <– PC + 4

- Physical Register Transfers

inst	Physical Register Transfers
	IR <– MEM[pc]
SW	A<– R[rs]; B <– R[rt]
	S <– A + SignEx(Im16);
	MEM[S] <– B PC <– PC + 4

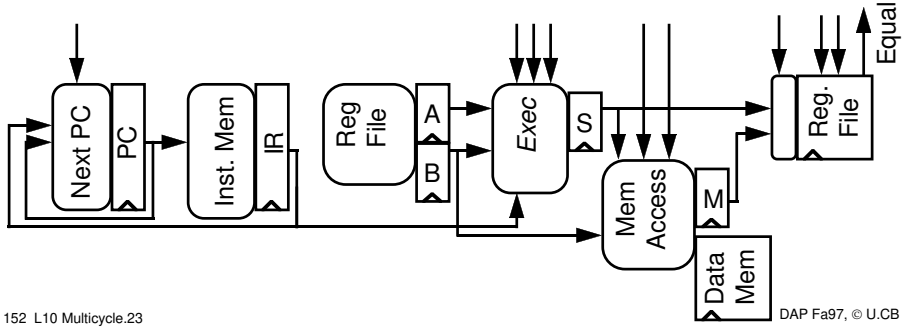

DAP Fa97, © U.CB

Step 4 : Branch

- Logical Register Transfer

inst	Logical Register Transfers
BEQ	if R[rs] == R[rt] then PC <= PC + sx(Im16) || 00 else PC <= PC + 4

- Physical Register Transfers

inst	Physical Register Transfers
	IR <– MEM[pc]
BEQ|$\overline{\text{Eq}}$	PC <– PC + 4

inst	Physical Register Transfers
	IR <– MEM[pc]
BEQ|Eq	PC <– PC + sx(Im16) || 00

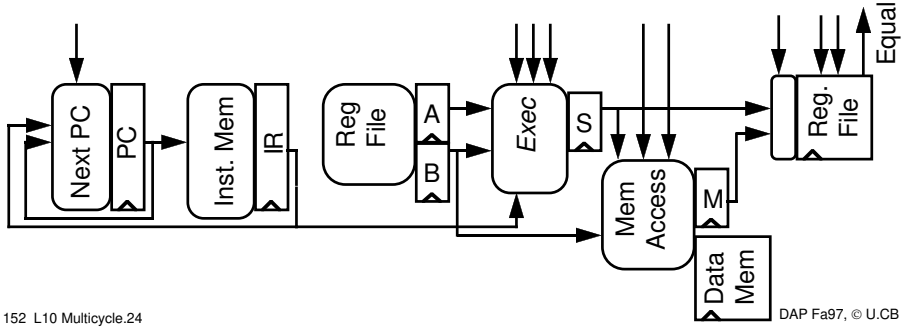

DAP Fa97, © U.CB

Alternative datapath (book): Multiple Cycle Datapath

- Miminizes Hardware: 1 memory, 1 adder

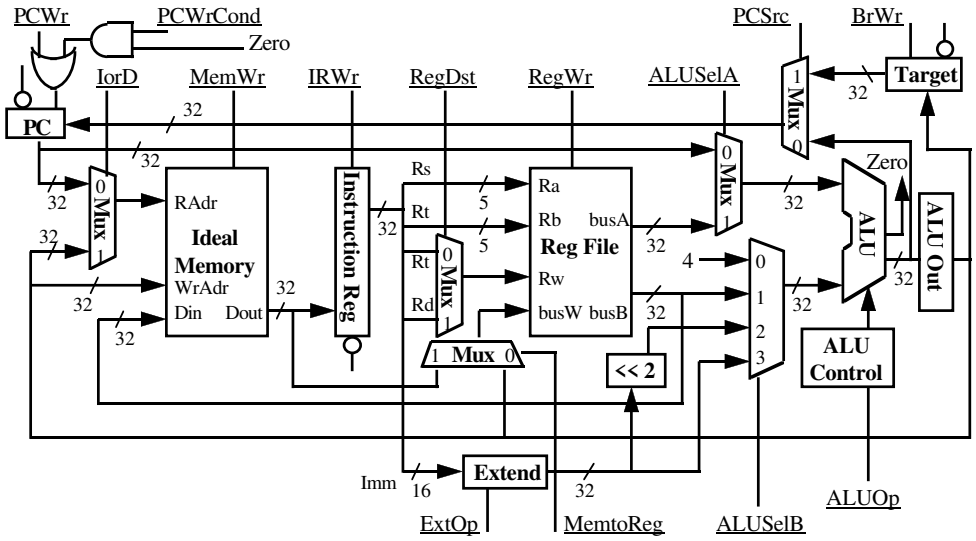

Our Control Model

- State specifies control points for Register Transfer
- Transfer occurs upon exiting state (same falling edge)

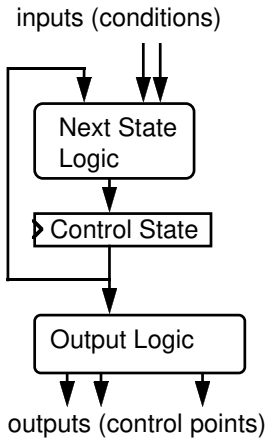

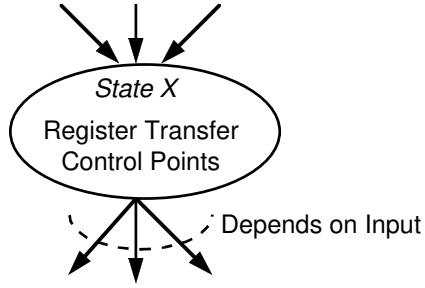

Step 4 => Control Specification for multicycle proc

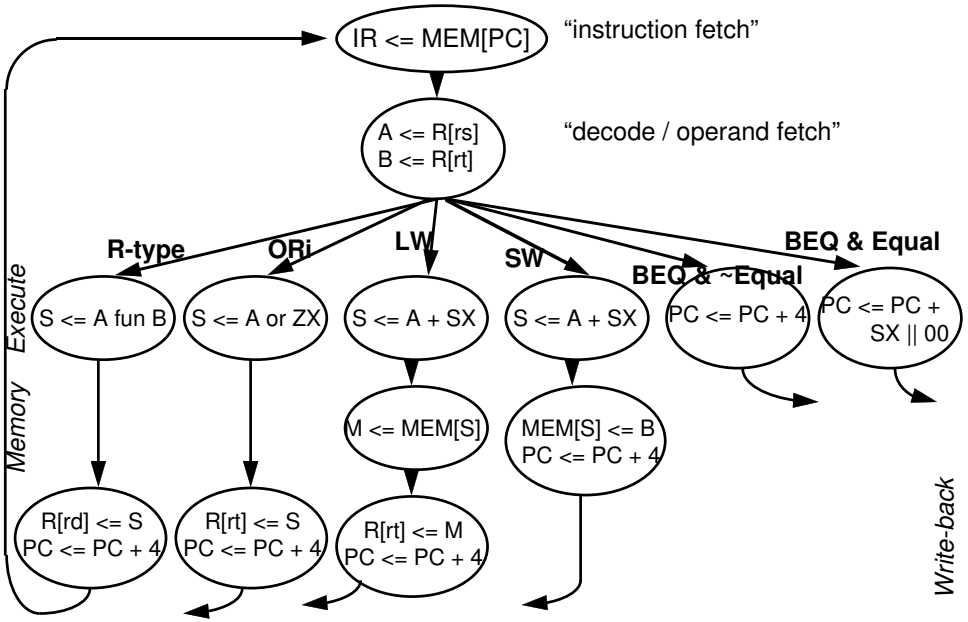

Traditional FSM Controller

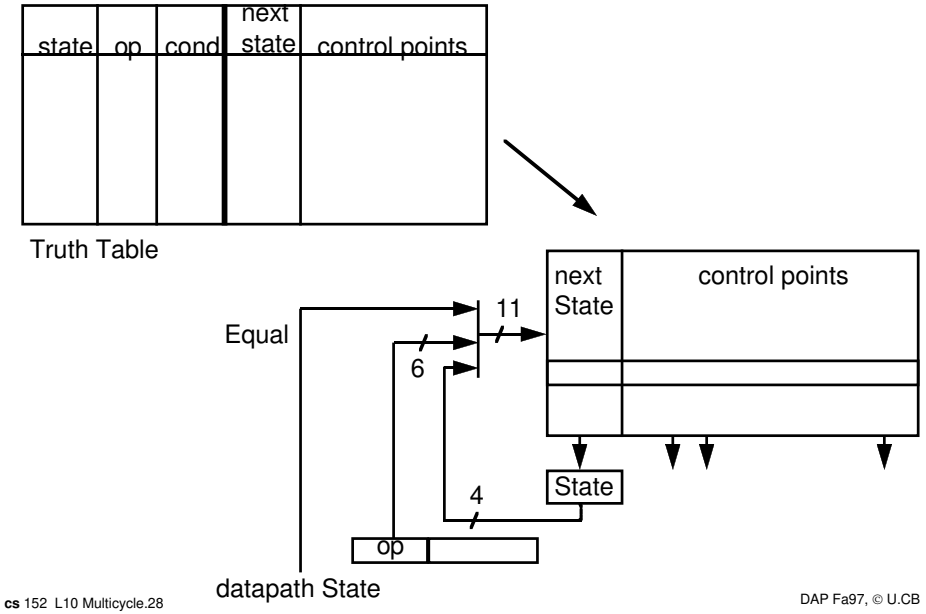

Step 5: datapath + state diagram => control

- Translate RTs into control points
- Assign states
- Then go build the controller

DAP Fa97, © U.CB

Mapping RTs to Control Points

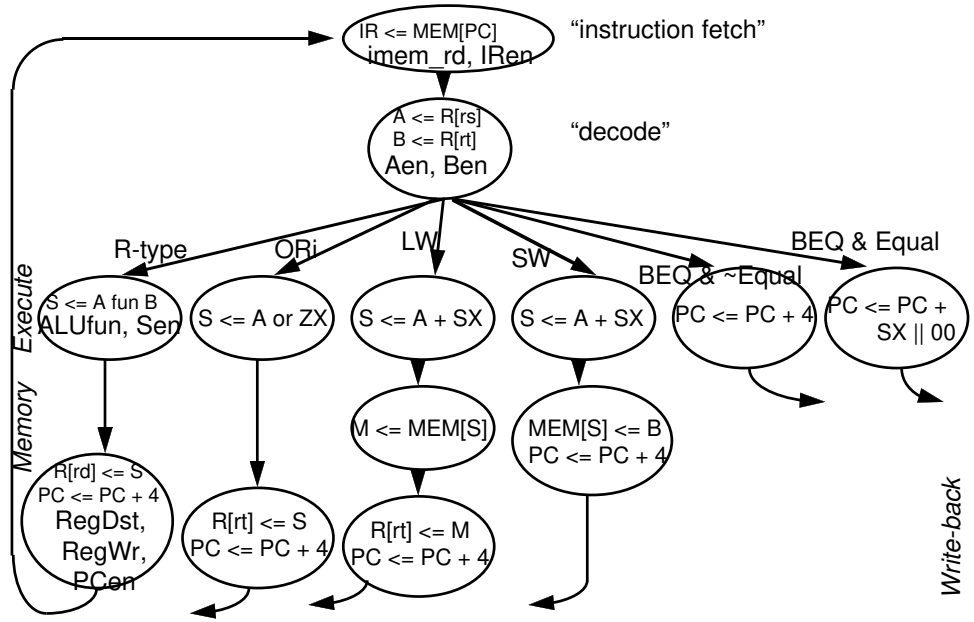

DAP Fa97, © U.CB

Assigning States

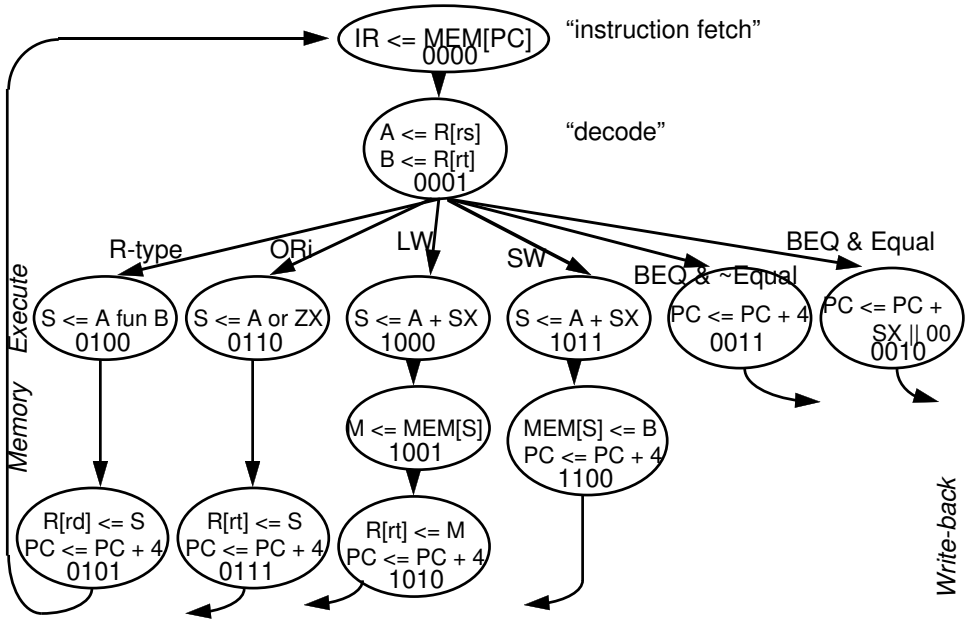

DAP Fa97, © U.CB

Detailed Control Specification

	State	Op field	Eq	Next	IR	PC en sel	Ops A B	Exec Ex Sr ALU S	Mem R W M	Write-Back M-R Wr Dst
	0000	??????	?	0001	1					
	0001	BEQ	0	0011			1 1			
	0001	BEQ	1	0010			1 1			
	0001	R-type	x	0100			1 1	*-all same in Moore machine*		
	0001	orI	x	0110			1 1			
	0001	LW	x	1000			1 1			
	0001	SW	x	1011			1 1			
	0010	xxxxxx	x	0000		1 1				
	0011	xxxxxx	x	0000		1 0				
R:	0100	xxxxxx	x	0101				0 1 fun 1		
	0101	xxxxxx	x	0000		1 0				0 1 1
ORi:	0110	xxxxxx	x	0111				0 0 or 1		
	0111	xxxxxx	x	0000		1 0				0 1 0
LW:	1000	xxxxxx	x	1001				1 0 add 1		
	1001	xxxxxx	x	1010					1 0 0	
	1010	xxxxxx	x	0000		1 0				1 1 0
SW:	1011	xxxxxx	x	1100				1 0 add 1		
	1100	xxxxxx	x	0000		1 0			0 1	

DAP Fa97, © U.CB

Performance Evaluation

- **What is the average CPI?**
  - **state diagram gives CPI for each instruction type**
  - **workload gives frequency of each type**

Type	CPI_i for type	Frequency	CPI_i x $freq_i$
Arith/Logic	4	40%	1.6
Load	5	30%	1.5
Store	4	10%	0.4
branch	3	20%	0.6
		Average CPI:	4.1

DAP Fa97, © U.CB

Controller Design

- **The state digrams that arise define the controller for an instruction set processor are highly structured**
- **Use this structure to construct a simple "microsequencer"**
- **Control reduces to programming this very simple device**
  - **microprogramming**

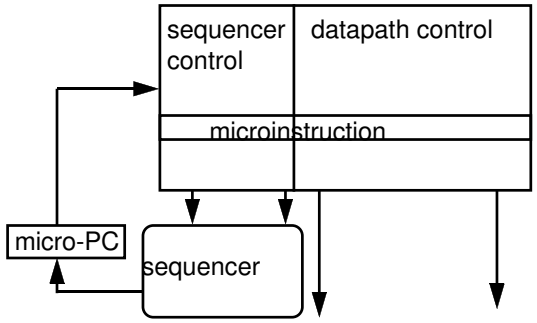

DAP Fa97, © U.CB

Example: Jump-Counter

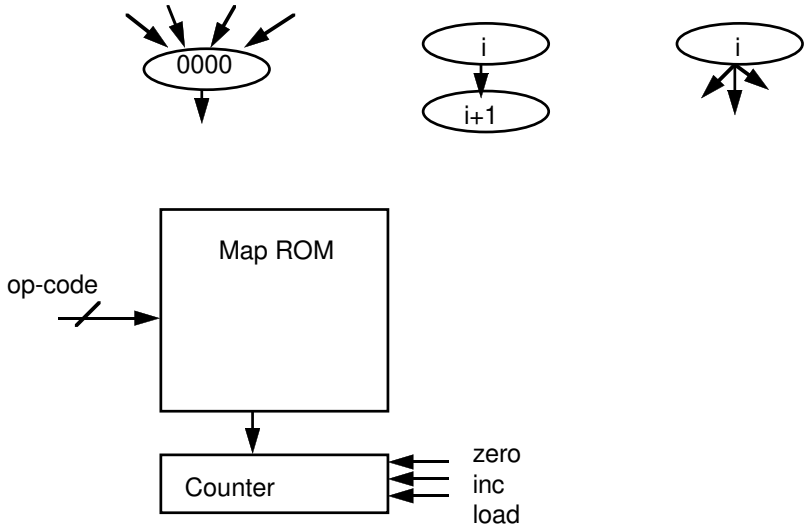

DAP Fa97, © U.CB

Using a Jump Counter

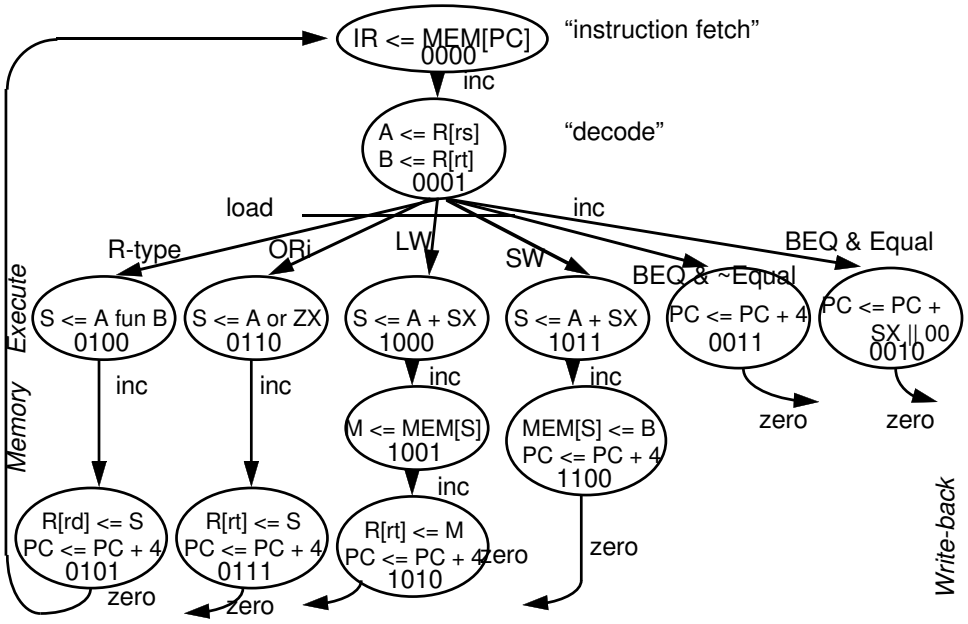

DAP Fa97, © U.CB

Our Microsequencer

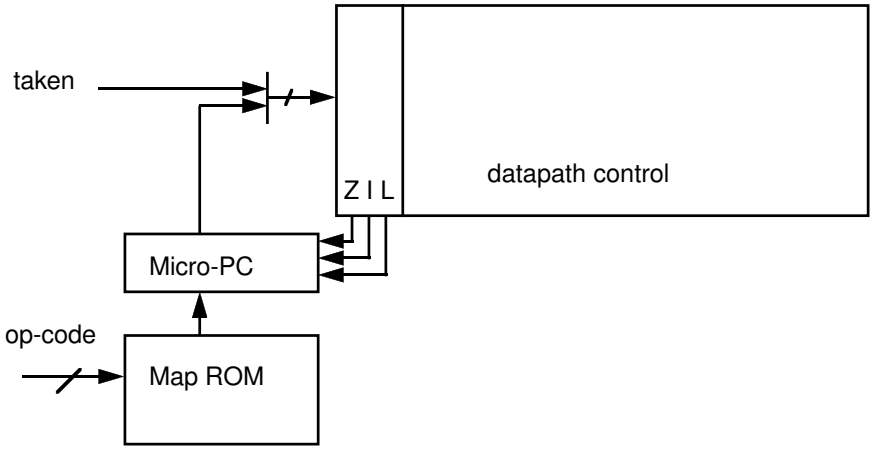

DAP Fa97, © U.CB

Microprogram Control Specification

	µPC	Taken	Next	IR	PC en	PC sel	Ops A	Ops B	Exec Ex	Exec Sr	Exec ALU	Exec S	Mem R	Mem W	Mem M	Write-Back M-R	Write-Back Wr	Write-Back Dst
	0000	?	inc	1														
	0001	0	load															
	0001	1	inc															
	0010	x	zero		1	1												
BEQ	0011	x	zero		1	0												
R:	0100	x	inc						0	1	fun	1						
	0101	x	zero		1	0										0	1	1
ORi:	0110	x	inc						0	0	or	1						
	0111	x	zero		1	0										0	1	0
LW:	1000	x	inc						1	0	add	1						
	1001	x	inc										1	0	0			
	1010	x	zero		1	0										1	1	0
SW:	1011	x	inc						1	0	add	1						
	1100	x	zero		1	0							0	1				

DAP Fa97, © U.CB

Mapping ROM

R-type	000000	0100
BEQ	000100	0011
ori	001101	0110
LW	100011	1000
SW	101011	1011

DAP Fa97, © U.CB

Example: Controlling Memory

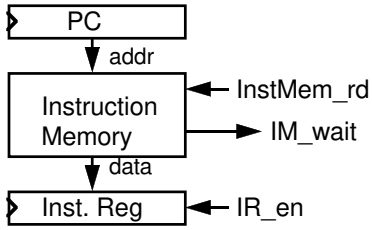

DAP Fa97, © U.CB

Controller handles non-ideal memory

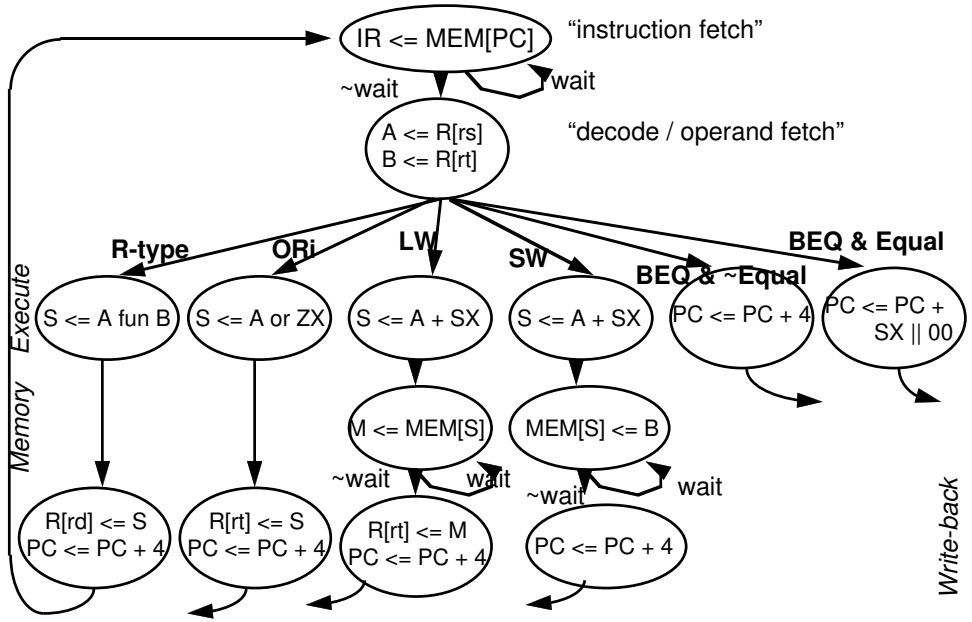

DAP Fa97, © U.CB

Really Simple Time-State Control

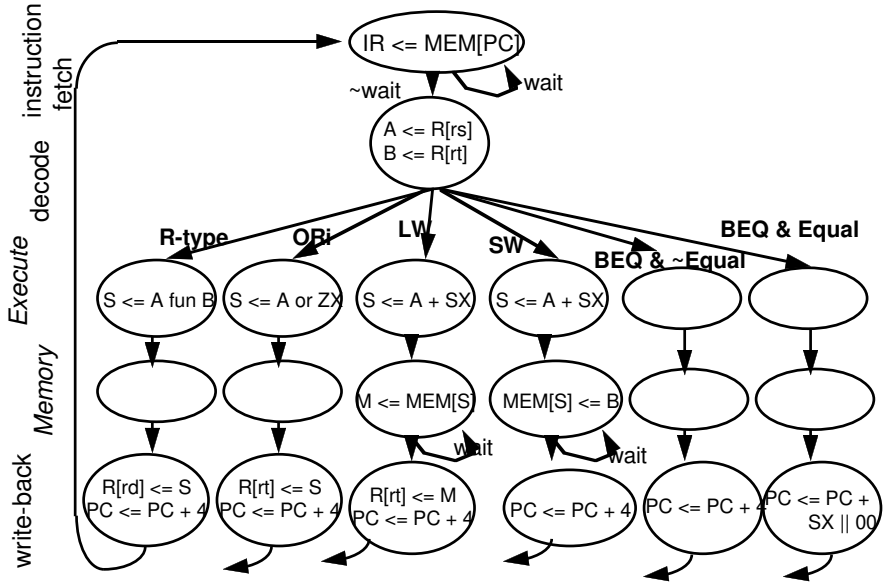

DAP Fa97, © U.CB

Time-state Control Path

° Local decode and control at each stage

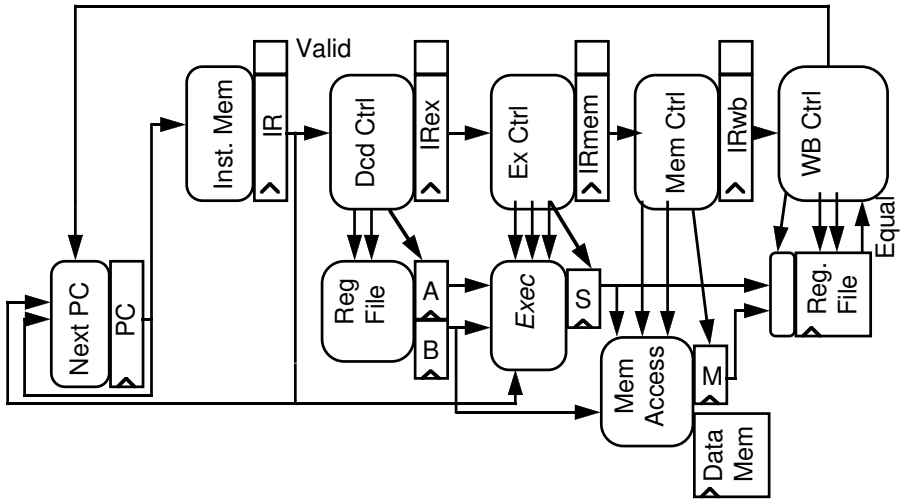

DAP Fa97, © U.CB

Overview of Control

° Control may be designed using one of several initial representations. The choice of sequence control, and how logic is represented, can then be determined independently; the control can then be implemented with one of several methods using a structured logic technique.

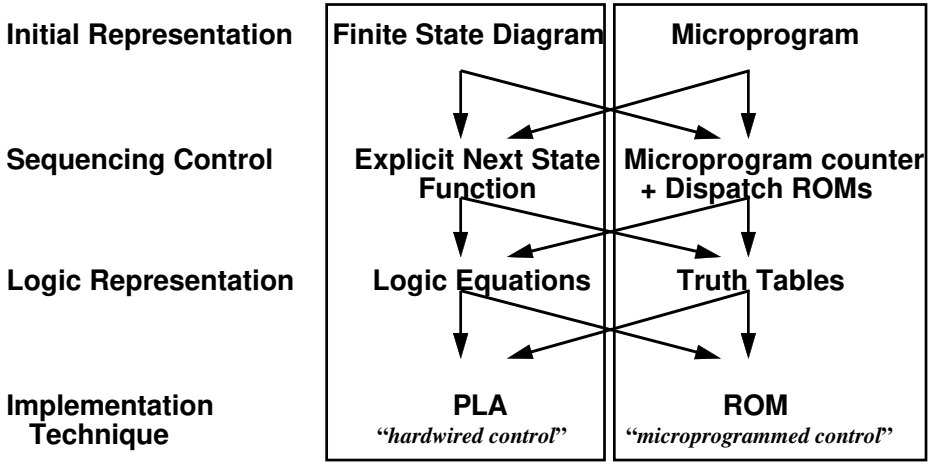

DAP Fa97, © U.CB

Summary

- Disadvantages of the Single Cycle Processor
  - Long cycle time
  - Cycle time is too long for all instructions except the Load
- Multiple Cycle Processor:
  - Divide the instructions into smaller steps
  - Execute each step (instead of the entire instruction) in one cycle
- Partition datapath into equal size chunks to minimize cycle time
  - ~10 levels of logic between latches
- Follow same 5-step method for designing "real" processor

Summary (cont'd)

- Control is specified by finite state digram
- Specialize state-diagrams easily captured by microsequencer
  - simple increment & "branch" fields
  - datapath control fields
- Control design reduces to Microprogramming
- Control is more complicated with:
  - complex instruction sets
  - restricted datapaths (see the book)
- Simple Instruction set and powerful datapath => simple control
  - could try to reduce hardware (see the book)
  - rather go for speed => many instructions at once!

Where to get more information?

- Next two lectures:
  - Multiple Cycle Controller: Appendix C of your text book.
  - Microprogramming: Section 5.5 of your text book.
- D. Patterson, "Microprograming," Scientific America, March 1983.
- D. Patterson and D. Ditzel, "The Case for the Reduced Instruction Set Computer," Computer Architecture News 8, 6 (October 15, 1980)